

EEE334

Lab #7 (Honors Lab)

Design an Audio Amplifier using MOS transistor

1 May 2020

Vincent Li

Dr. Allee

Introduction:

The goal of this experiment is to design a multistage audio amplifier with MOS transistors. The only equipment needed is LTSpice.

The design requirements are: overall voltage amplification $A_V \geq 300V/V$, total power consumption $P_{TOT} \leq 200mW$, load resistance $1k\Omega \leq R_L \leq 1M\Omega$, bandwidth is between $f_L \leq 20Hz$ and $f_H \leq 20kHz$, and source voltage $V_S \leq 5mV_{pp}$.

Voltage gain, MOS technology, transient analysis, and frequency response analysis will be researched.

Equipment and Components:

Equipment:

Name	Model	Quantity
LTSpice		


Components:

Name	Value	Quantity
v_s	sine $0.0025V_{amp}$	1
V_{DD}	$12V$	1
NMOS transistor $0.8\mu m$ tech	$k_n = 0.127mA/V^2$ $V_t = 0.7V, \lambda = 0.001$ $\frac{W}{L} = 3$	4
Capacitor C_{f1}	$8\mu F$	1
Capacitor C_{f2}	$8nF$	1
Resistor R_{f1}	$1k\Omega$	1
Resistor R_{f2}	$1k\Omega$	1
Resistor R_{GA}	$2.6M\Omega$	4
Resistor R_{GB}	$1M\Omega$	4
Resistor R_{D1-3}	$6.6k\Omega$	3
Resistor R_{D4}	$5.3k\Omega$	1
Resistor R_S	3Ω	3
Capacitor C_S	$50\mu F$	3
Capacitor C	$1\mu F$	5
Resistor R_L	$1M\Omega$	1

Procedure:

1. Design a band-pass filter for v_s to fulfill the bandwidth requirement.

Figure 1: Schematic of the band-pass filter

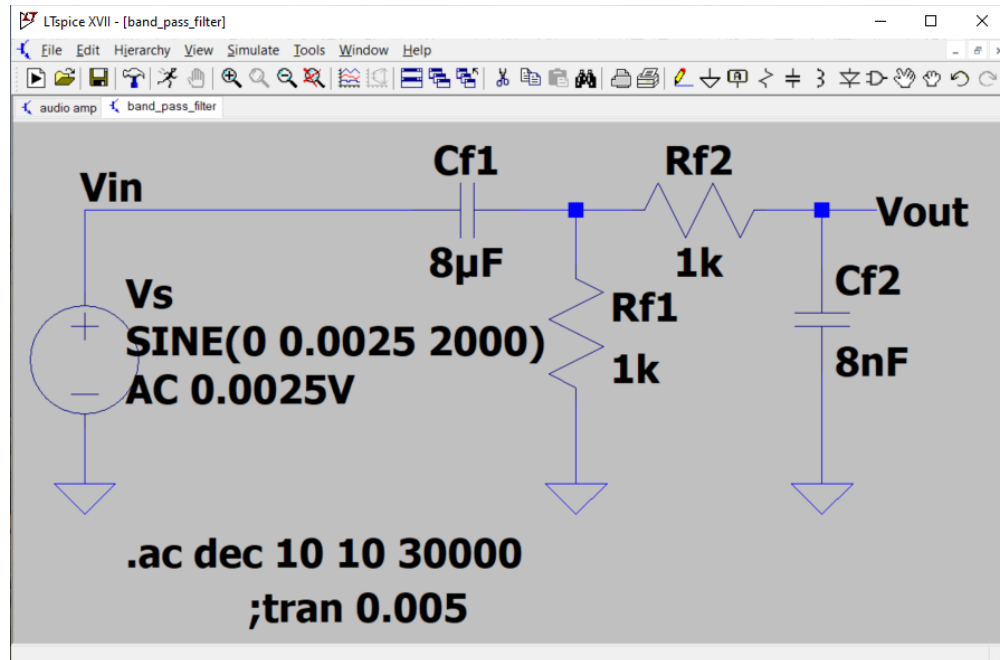

$$\text{Let } R_{f1} = R_{f2} = 1k\Omega$$


$$f_L = 20Hz, f_H = 20kHz$$

$$C_{f1} = \frac{1}{2\pi f_L R_{f1}} = \frac{1}{2\pi * 20 * 1000} = 7.958 * 10^{-6} \approx 8\mu F$$

$$C_{f2} = \frac{1}{2\pi f_H R_{f2}} = \frac{1}{2\pi * 20000 * 1000} = 7.958 * 10^{-9} \approx 8nF$$

2. Design a single-stage NMOS common-source amplifier.

Figure 2: Schematic of NMOS amplifier for stages 1-3

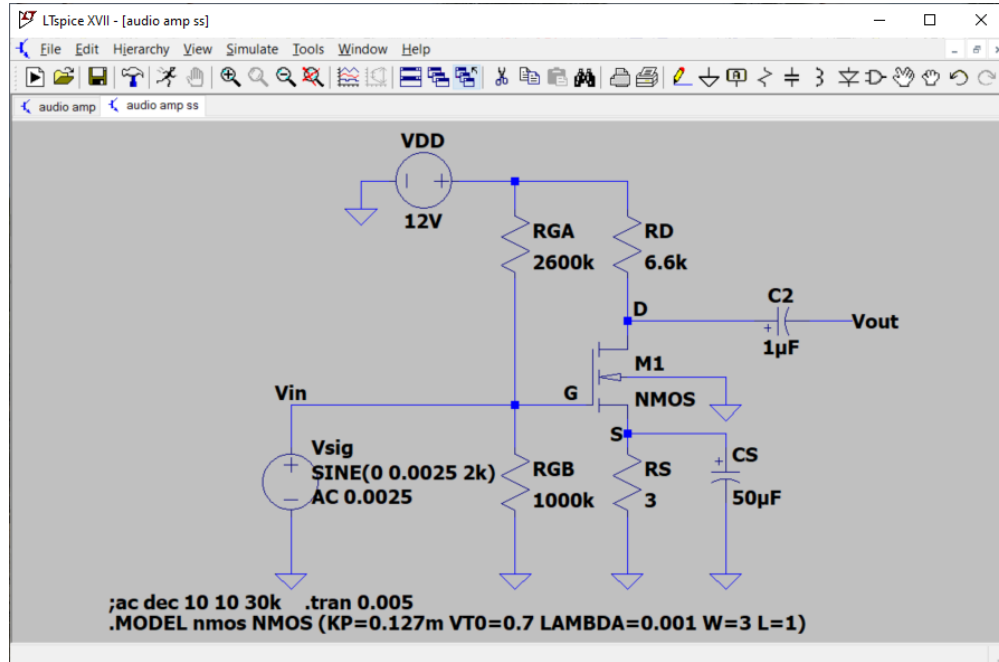

In saturation region: $V_{DS} \geq V_{GS} - V_t$; $V_D \geq V_G - 7$; $V_t = 0.7V$

To bias, let $V_G = 3.333V$

$$V_G = V_{DD} * \frac{R_{GB}}{R_{GA} + R_{GB}} = 3.333 = 12 * \frac{R_{GB}}{R_{GA} + R_{GB}}$$

$$3.333(R_{GA} + R_{GB}) = 12 * R_{GB}; 3.333R_{GA} + 3.333R_{GB} = 12R_{GB}$$

$$3.333R_{GA} = 8.667R_{GB}$$

$$R_{GA} = 2.600R_{GB}; \frac{R_{GA}}{R_{GB}} = \frac{1}{2.600}$$

Have $R_{GA} = 1M\Omega$, $R_{GB} = 2.6M\Omega$

Let $V_D = 3.279V$, just a bit less than V_G

Let $V_S = 0.004V$ which is very small

$$\frac{V_{DD} - V_D}{R_D} = \frac{V_S}{R_S}; \frac{12 - 3.279}{R_D} = \frac{0.004}{R_S}; \frac{8.721}{R_D} = \frac{0.004}{R_S}; \frac{8.721}{0.004} = \frac{R_D}{R_S}$$

$$\frac{R_D}{R_S} \approx \frac{6.6k}{3}, \text{ choose 3 for practical purposes}$$

$$R_D = 6.6k\Omega, R_S = 3\Omega$$

Add a $50\mu F$ capacitor at the source to further increase gain.

Add a **1 μ F** capacitor at the output to remove DC from it. The capacitance just needs to be large enough to block DC.

3. Cascade this single-stage amplifier 3 times to get triple the gain.
4. Design a fourth single-stage amplifier with a less gain compared to the previous. Otherwise, cascading the first single-stage amplifier 4 times will skew the output waveform severely and the overall voltage gain will be impractically high.

Have the same design as the previous single-stage amplifier, but without R_S and C_S .

Let $V_G = 3.333V$, so $R_{GA} = \mathbf{2.6M\Omega}$ and $R_{GB} = \mathbf{1M\Omega}$

Let $V_D = 4.964V$, just under $5V$, which is the V_{DD} of the NMOS

R_D and I_D can be $I_D * R_D = 5 - 4.964 = 0.036V$

$$1.328mA * 5.3k\Omega = 0.036V$$


$$\mathbf{R_D = 5.3k\Omega}$$

Add a **1 μ F** capacitor at the output. The capacitance just needs to be large enough to block DC.

5. Let $R_L = \mathbf{1M\Omega}$, which is the highest allowed value.

Results:

Figure 3: Schematic of the complete audio amplifier circuit

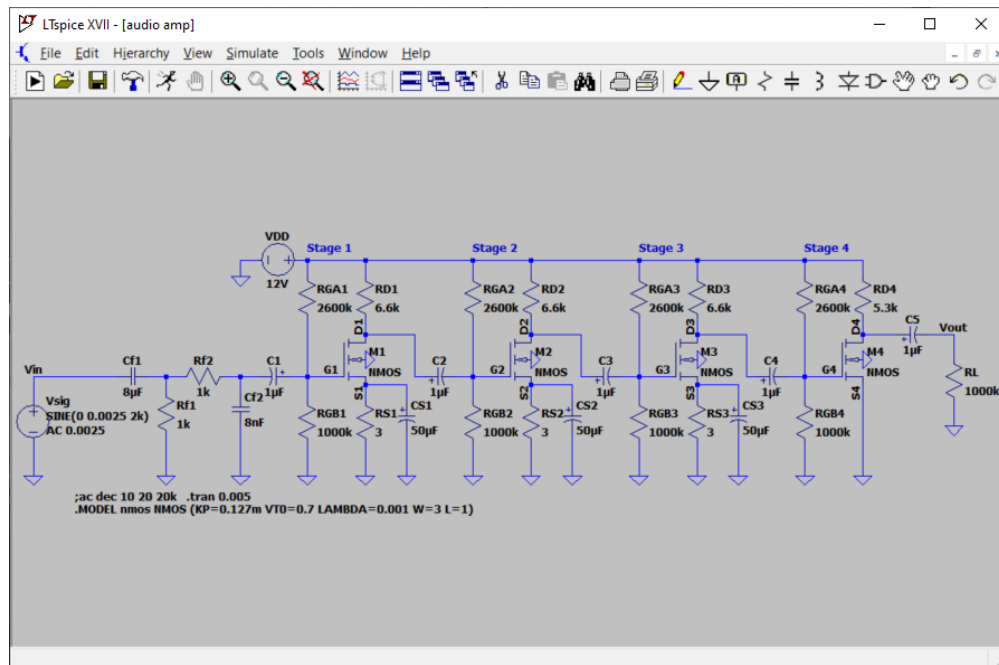

Circuit parameters:

V_{DD}	12V
V_{SS}	0V (ground)
NMOS $\frac{W}{L}$	3/1
NMOS technology	$0.8\mu m$ ($V_t = 0.7V, k_n = \frac{0.127mA}{V^2}$)
NMOS λ	0.001
Load resistance	1M Ω

*all MOSFETs used have the same parameters

Figure 4: Transient analysis of the first stage

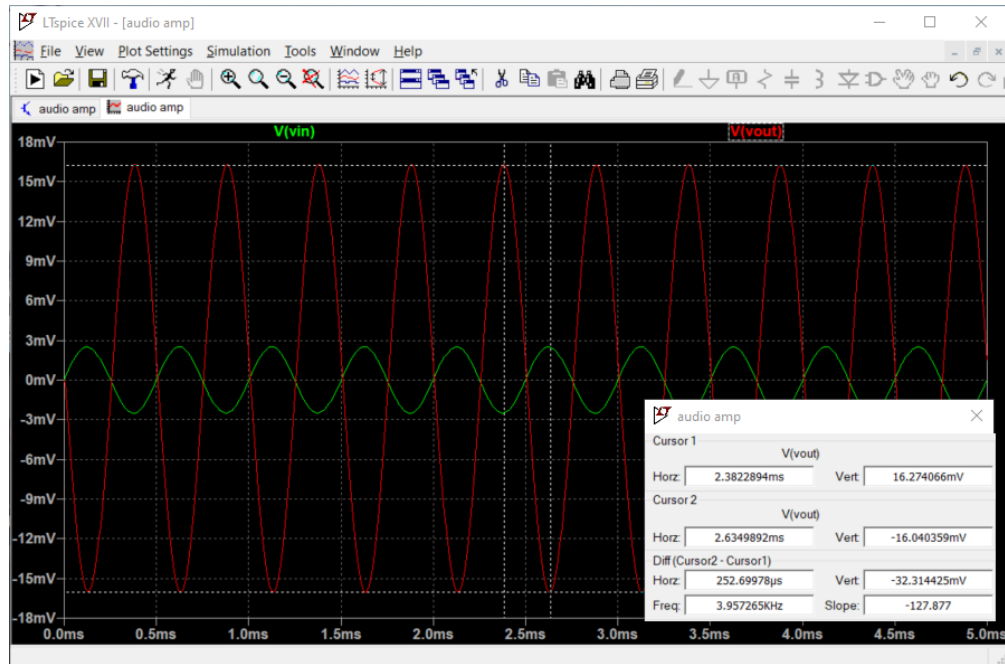


Figure 5: Transient analysis for stage 4


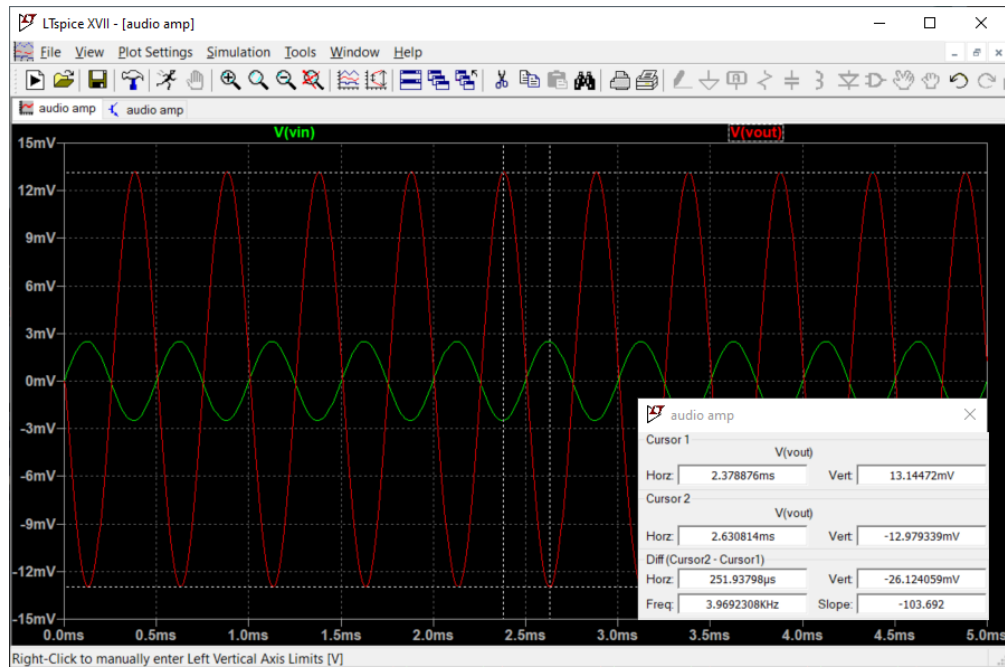



Figure 6: Transient analysis of the entire circuit

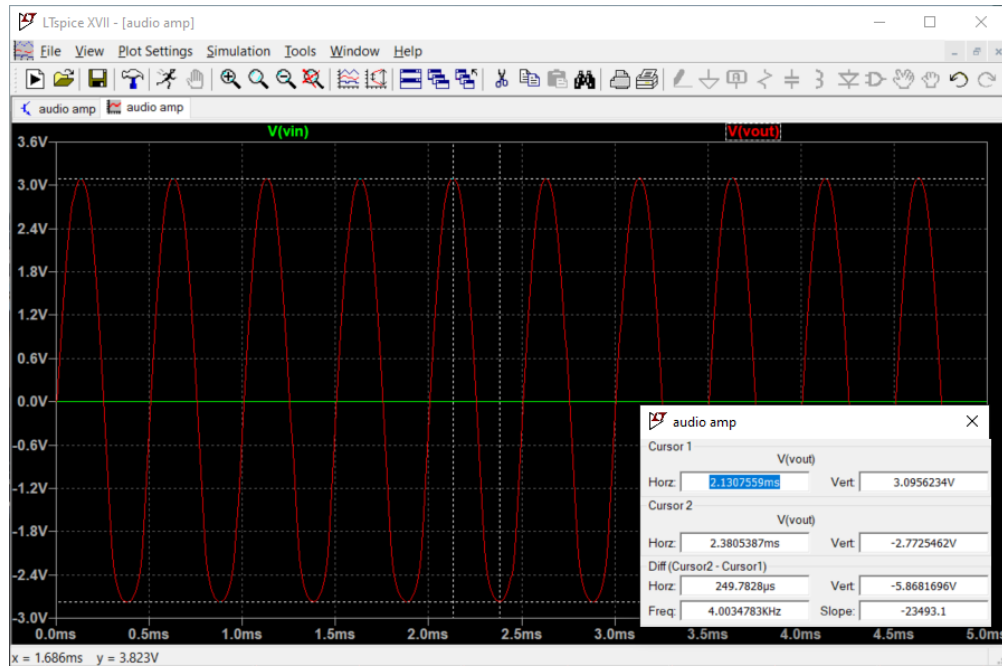

$$v_{out\ pp} = 5.869V$$

$$A_v = \frac{v_{out\ pp}}{v_{in\ pp}} = \frac{5.869}{0.005} = 1173.8V/V \geq 300V/V$$

Figure 7: Frequency analysis of the entire circuit

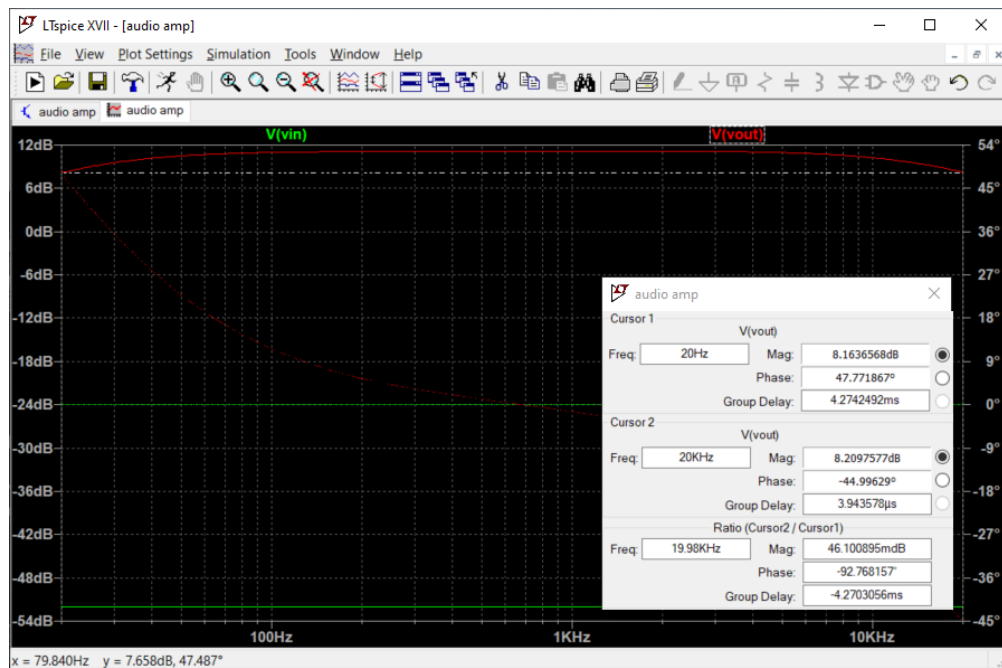


At $f_L = 20\text{Hz}$, $v_{out} = 8.164\text{dB}$

At $f_H = 20\text{kHz}$, $v_{out} = 8.210\text{dB}$

Highest magnitude = 11.182dB at 1.255kHz

Figure 8: Total power consumption

 

Discussion:

The complete schematic of the audio amplifier is in Figure 3. In summary, it has a band-pass filter at the signal input, 3 of the same stages, a 4th different stage, and each stage is RC-coupled. All stages have the same specification NMOS ($0.8\mu\text{m}$ technology) and all are common source amplifiers. $V_{DD} = 12\text{V}$ and V_{SS} is grounded (0V). I chose λ to be 0.001 and W/L to be 3. The load resistance is $1\text{M}\Omega$, which is the highest allowed value.

The input signal is $0.005V_{pp}$ and the output signal is $5.869V_{pp}$, so the amplifier yields an overall voltage gain of 1173.8V/V which is greater than the minimum required gain of 300V/V . For the first, second, and third stages, the voltage gain is 6.463V/V , and for the final stage, the voltage gain is 5.225V/V . These values were calculated using the transient analysis from Figures 4-6.

From the frequency analysis (Figure 7), we learn that at 20Hz , which is the required max f_L , the magnitude of the output voltage is 8.164dB . At 20kHz , which is the required minimum f_H , the magnitude of the output signal is 8.210dB . Through a quick scan of the analysis graph, the highest magnitude is 11.182dB . Since $11.182 - 8.164 = 3.022\text{dB} \approx 3\text{dB}$

and $11.182 - 8.210 = 2.982\text{dB} \leq 3\text{dB}$, then bandwidth is at least between 20Hz and 20kHz . Although 3.022dB isn't exactly less than or equal to 3dB , the difference is very small.

Finally, the total power consumption is less than 200mW , as shown in Figure 8.

While designing the circuit, I had to deliberately choose λ and $\frac{W}{L}$. Additionally, for each stage, I picked the desired V_G , V_S , V_D , and I_D in order to get the correct resistor values. I found that having gate voltage and drain voltage very similar while staying in the saturation region provided a more ideal voltage gain. I also choose the values of R_L , V_{DD} , and V_{SS} . For the capacitors between the stages they simply had to be large enough to block DC voltage, but I noticed that for stages 1-3, adjusting the C_S to $50\mu\text{F}$ increased voltage gain. I also decided to use only NMOS transistors because I read that they are quicker than PMOS ones.

Conclusion:

In this experiment, I learned how to design a multi-stage MOSFET amplifier from scratch, which involved choosing the gate, source, drain voltages, and drain current to get an appropriate voltage gain from each stage, and then coupling them together to satisfy the voltage gain requirement. Difficulties included deciding the correct type of amplifier (common source), choosing the right layout of the stage (which components go where), choosing the best assumed values to start with, and tweaking capacitor values on LTSpice to see how the voltage gain responded from those changes. The goal of this lab was achieved.

Post-lab Questions:

1. The advantages of using multistage amplifiers as opposed to single-stage amplifiers includes being able to achieve a very high gain, power efficiency, and being able to design properties like input and output resistance. The disadvantages are that they are more expensive and more complex to design.
2. If V_{DD} and V_{SS} were 10V , then the overall voltage gain would decrease. Additionally, gate and drain voltage will decrease.
3. If the overall voltage amplification was increased to 500V/V , this design would fulfill this new requirement.